 


**Main Objective:**

- 1) To enhance your ability to code Hierarchical Circuits in VHDL.**
- 2) To verify (using simulation) the timing of various Addition Circuits.**

Start the program ModelSim. **Create a new folder** to store your project files before creating a new project (called "LWS02"). **Create a file called LuckyGates.vhd**. When the "create" window appears you should **add the existing file** called "LuckyGates.vhd". **Compile the code** so that the entities appear in the Work Library. Check that the **ENTITIES** are now inside the Work library.

The following questions require that you create structural descriptions for various circuits. The circuits are to be built from the following primitive gates.



I have already created the **ENTITY/ARCHITECTURE** definitions for these objects in a file called "LuckyGates.vhd". You should build your **ENTITIES** from these primitive gates. **DO NOT use VHDL operators** to create basic gates.

**Please demonstrate to the Teaching Assistant the following.**

**FOR PART 1:** (deadline: beginning of Lab on Feb 7<sup>th</sup> 2020)

Chain1: VHDL architecture / Circuit Diagram (drawn in your lab notebook)

Tree1: VHDL architecture / Circuit Diagram

Chain2: VHDL architecture / Circuit Diagram

Tree1: VHDL architecture / Circuit Diagram

Simulation results showing the output signal waveforms of all four circuits in ONE diagram.

**FOR PART 2:** (deadline: beginning of Lab on Feb 14<sup>th</sup> 2020)

Ripple: VHDL architecture / Circuit Diagram and waveforms with expanded sum bits.

BookSkip: VHDL architecture / Circuit Diagram and waveforms with expanded sum bits.

GoodSkip: VHDL architecture / Circuit Diagram and waveforms with expanded sum bits.

Brent-Kung: VHDL architecture / Circuit Diagram and waveforms with expanded sum bits.

Table of predicted and measured timing. (drawn in your lab notebook)

All circuit diagrams must be complete **showing every element** of the VHDL architecture.

- All internal signals must be **labelled identically** to the VHDL code.
- **Do not omit elements** simply because a structure is repetitive.
- If the circuit is **recursive** you should draw TWO circuit diagrams; one for the **recursive pattern** and one for the **stopping condition**. Both circuits should be **labelled identically to your VHDL code**.

Please refer to the Handout-10-252-1167.pdf for further information hierarchical circuit descriptions.

PART 1:1) Writing multiple ARCHITECTUREs for a single ENTITY.



We can include more than one **ARCHITECTURE** for a single **ENTITY** in a file. To accomplish this we simply write the extra **ARCHITECTUREs** after the **ENTITY** giving each **ARCHITECTURE** a unique name.

We specify the desired **ARCHITECTURE** each time that we instantiate the **ENTITY** by placing the **ARCHITECTURE** name inside parentheses.

ie.

```
c1: entity      Work.MyEntity( FirstArchitectureName )  port map ( ... );
c2: entity      Work.MyEntity( SecondArchitectureName) port map ( ... );
```

- Using the **ENTITY**, “ParityCheck” that I have supplied in a file called “Part1.vhd”, **Create two** architectures called “tree1” and “chain1” according to the following diagrams.
- Simulate your designs** for 700 nsec using the testbench file “TestPart1.vhd”. If you are convinced that the **ARCHITECTUREs** are correct then submit your circuit diagrams, VHDL code.

  PART 1: 1) Continued

## 2) Generating repetitive structures during elaboration.

The VHDL compiler can be instructed to create many concurrent statements using a **GENERATE** statement. (google “VHDL generate”) The code that I have provided also contains examples demonstrating the use of **GENERATE** statements.


- a) **Create** a third **ARCHITECTURE** for the xor chain. Use a **GENERATE** statement to build a third **ARCHITECTURE** for the **ENTITY** ParityCheck.  
Call this new **ARCHITECTURE** “chain2”

- b) **Add an instance** of this new **ARCHITECTURE** to the testbench file “TestPart1”.  
**Run the simulation** and verify that the signals Chain1Out and Chain2Out are identical.

Notice that the **ENTITY** declaration for ParityCheck contains a clause **GENERIC** by it's **PORT** definition. The **GENERIC** clause is a way to pass values to instances of an **ENTITY**. The value specified in the **ENTITY declaration** is simply the default value of the **GENERIC** parameter. We pass a specific value of the parameter to an **ENTITY** object whenever we instantiate the **ENTITY**.

ie.      c1: entity Work.MyEntity(MyArchitecture) generic map (MyValues) port map ( ... );

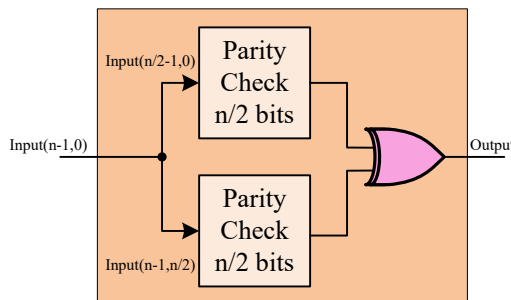- c) **Build a recursive ARCHITECTURE** of the ParityCheck ENTITY called “Tree2”. We shall define this **ARCHITECTURE** recursively. Here is the idea. a parity check of width 32 can be determined by xoring two parity checks of width 16.




Inside the **ARCHITECTURE** for **ENTITY** ParityCheck, **instantiate** two instances of **ENTITY** ParityCheck. Make sure that these two instances are of half the width by passing a value to the **GENERIC** parameter. Then **produce the output** with an instance of an xor2 **ENTITY**. **Add a conditional GENERATE** statement around these instantiations to prevent them from elaborating when the parameter is becomes too small. You should try 3 or Less. Finally, **add two conditional GENERATE** statements that instantiate correct NON-recursive **ENTITY**s for the cases when the **GENERIC** parameter is either 3 or 2. Be careful when dividing the parameter by 2. Integer division truncates. It is also possible to use a width = 1 as a stopping condition. Does this work?


- d) **Add an instance** of this new **ARCHITECTURE** to the testbench. Make sure that the **ENTITY** is passed a width of 8. **Run the simulation** and check that we have the same result as Tree1Out.
- e) **Submit** the **waveform** window that shows the results of all **ARCHITECTURE**s.  
**Submit** your **Circuit Diagrams** and **VHDL code** in the file "Part1.vhd". **Submit fully labelled circuit diagrams** for all four **ARCHITECTURE**s. DO NOT expanded the circuit diagram for the Recursively defined circuit. **Your circuit diagrams should match EXACTLY to the lines of your VHDL code.**

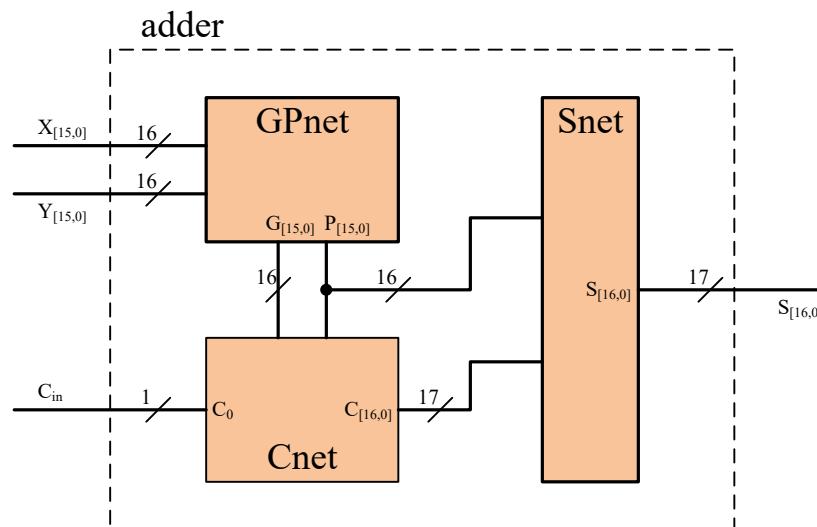**PART 2:**3) **Addition Circuits.**


We are now going to study techniques for **designing addition circuits**. I have provided the basic structure of the circuit in the file “part2.vhd”. **Read this file carefully** and make sure that you understand the code. You are expected to be able to create this code yourself. The file “part2.vhd” declares an **ENTITY adder16** and then provides a structural description that places three **ENTITY**s inside the **ARCHITECTURE**. The **GPnet** and **Snet** **ENTITY/ARCHITECTURE**s are provided inside the file “Part2.vhd”. Note the use of **GENERATE** statements.



 - a) **Add the file** “Cnet.vhd” to your project. This file contains the **ENTITY** declaration for the carry network. **Design** an **ARCHITECTURE** called “Ripple” for a ripple carry network. You can find details from your Lecture Notes. I have included a simple building block **ENTITY** called “Cprop” that you should use for most of your Cnet **ARCHITECTURE**s. You should also **declare an internal signal** of type std\_logic\_vector to connect the carries. This signal will be useful in other **ARCHITECTURE**s.



 - b) Now **add the file** “TestPart2.vhd” to your project and **compile the code**. An **ENTITY** called TestPart2 should now be in the Work Library. This file instantiates the **ENTITY** adder and tests the design by stimulating the inputs with various values of the operands. **Start a new simulation** and select the TestPart2 **ENTITY** from the Work Library. Add all the signals in the region to the wave window and then **run a simulation** for 350 ns. **Expand the Bits of signal SR** so that you can see the detailed timing of the carry propagation. **Submit** the waveform.
- c) Now it is time to compare the ripple network design to a skip network design. **Build** a 16-bit carry network with a skip path for every 4-bits. The design of a block of 4-bits is given in Parhami, page 183, Figure 10.7. Try implementing skip blocks using the Cprop **ENTITY** as shown below. Call the **ARCHITECTURE** “BookSkip”



- d) **Run the simulation** of TestPart2 again. This time you should see waveforms for both SR and SBS signals. Expand the bits of these signals and **compare** them to see if the skip paths are working correctly. You should find that the improvement is minimal. You can verify that the skip paths are working correctly by checking bits 4, 8, 12 & 16. There is a flaw in the design. **Submit** the simulation waveform with the bits of SBS expanded.
- e) You now need to **correct the error** in the design. This involves adding a few more “or2” **ENTITY**s. **Create a new ARCHITECTURE** called “GoodSkip”. You may find it easy to simply copy & paste the BookSkip **ARCHITECTURE** and then edit the copy.
- f) **Run the simulation** again. You should see valid data on the signal line SGS. With the improvement that one would expect when using a skip trick.
- g) Finally **implement a Brent-Kung Look-Ahead** network (See Lecture Notes) using the recursive method of definition. ( You may assume that the width is a power of 2)
- h) The testbench simulates five additions. **Make a table** that has five rows, one for each addition. Label each row with the values of X, Y and  $C_{in}$ . The table should have four columns, one for each Cnet design. Enter both the **predicted** (from theory) and the **measured** (from simulation) **time delays** for output value to stabilize, for all circuits.